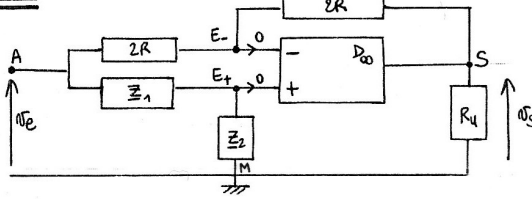


**EXE 5.9:**



1) loi des noeuds en Termes de Pot. en  $E_+$ :  
 $\frac{V_E - V_{E+}}{Z_1} + \frac{V_M - V_{E+}}{Z_2} + 0 = 0$  (1)  
 loi des noeuds en Termes de Pot. en  $E_-$ :  
 $\frac{V_E - V_{E-}}{2R} + \frac{V_S - V_{E-}}{2R} + 0 = 0$  (c)  
 (e)  $\Rightarrow V_S = 2V_{E-} - V_E$  (e)

(a)  $\rightarrow V_{E+} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right) = \frac{V_E}{Z_1} \rightarrow V_{E+} = \frac{Z_2}{Z_1 + Z_2} V_E$  (a)  
 AO en régime linéaire + AO idéal  $\Rightarrow$  donc  $V_{E+} = V_{E-}$   
 $V_S = \left( \frac{2Z_2}{Z_1 + Z_2} - 1 \right) V_E$  (e)

(e)  $\frac{V_S}{V_E} = \frac{Z_2 - Z_1}{Z_2 + Z_1} = H(j\omega)$


2)  $Z_1 = R$   $Z_2 = \frac{1}{jC\omega}$   $\rightarrow H(j\omega) = \frac{\frac{1}{jC\omega} - R}{\frac{1}{jC\omega} + R} = \frac{1 - jRC\omega}{1 + jRC\omega} = \frac{1 - j\alpha}{1 + j\alpha}$   
 $\alpha = \frac{\omega}{\omega_0}$   $\omega_0 = \frac{1}{RC}$

$G_{dB} = 20 \log |H(j\omega)| = 20 \log (1 + \alpha^2) - 20 \log (1 + \alpha^2) = 0$

$\phi = \arg H(j\omega) = \arg (1 - j\alpha) - \arg (1 + j\alpha) = \arctan \frac{-\alpha}{1} - \arctan \frac{+\alpha}{1}$


$G_{dB} = 0$   $\phi = \arg H = -2 \arctan \alpha$

**FILTRE DÉPHASEUR**

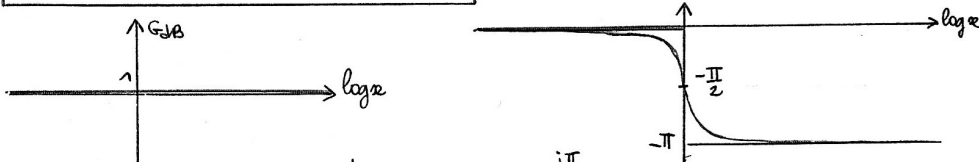


3)  $Z_1 = \frac{1}{jC\omega}$   $Z_2 = R \rightarrow H'(j\omega) = -H(j\omega) = e^{j\pi} H(j\omega)$

On tombe sur un filtre déphaseur différent:  $G'_{dB} = 0$   $\phi' = \arg H' = \pi - 2 \arctan \alpha$

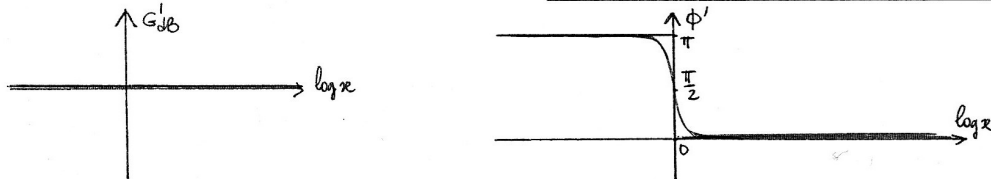

**EXE 5.10:**

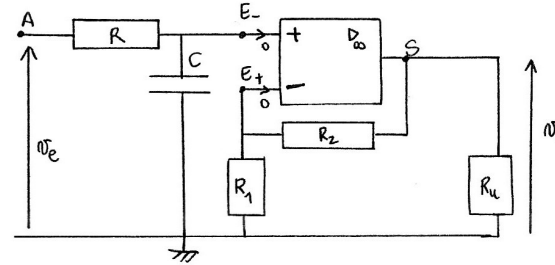

1) loi des Noeuds en T. de Pot. en  $E_-$ :  
 $\frac{V_E - V_{E-}}{R} + \frac{V_M - V_{E-}}{\frac{1}{C\omega}} = 0$  (a)  
 loi des N. en T. de Pot. en  $E_+$ :  
 $\frac{V_M - V_{E+}}{R_1} + \frac{V_S - V_{E+}}{R_2} = 0$  (e)  
 AO idéal:  $V_{E-} = V_{E+}$  (e)


(a)  $\rightarrow V_{E-} \left( \frac{1}{R} + jC\omega \right) = \frac{V_E}{R}$  (a) (e)  $\rightarrow V_{E+} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_S}{R_2}$  (e)

(e) (e)  $\rightarrow \frac{V_S}{R_2} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \rightarrow \frac{V_S}{V_E} = \frac{R_2}{R} \frac{R_1 + R_2}{R_1 R_2} \frac{1}{1 + jRC\omega} = \frac{R_1 + R_2}{R_1} \frac{1}{1 + jRC\omega}$

$H_0 \equiv \frac{R_1 + R_2}{R_1}$   $\omega_0 \equiv \frac{1}{RC} \rightarrow H(j\omega) = \frac{H_0}{1 + j\alpha}$  avec  $\alpha = \frac{\omega}{\omega_0}$   
 $\omega_c = \omega_0$  BP:  $[0, \omega_0]$

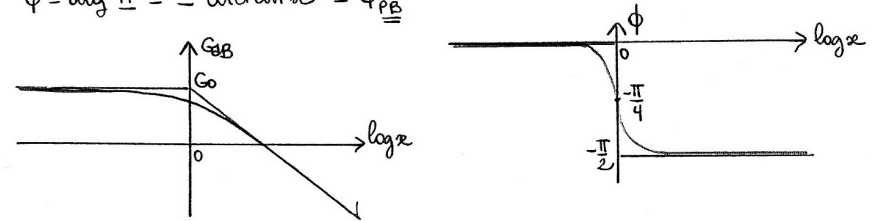2)  $G_{dB} = 20 \log H_0 - 20 \log (1 + \alpha^2) = G_0 + G_{dB PB}$

$\phi = \arg H = -\arctan \alpha = \phi_{PB}$



Pulsat° de Coupure  $G_{dB}(\omega_c) = G_{dB}(\max) - 3dB = G_0 - 3dB = G_0 - 10 \log (1 + \alpha^2)$   
 $\rightarrow \alpha_c = 1 = \frac{\omega}{\omega_0}$

3) On veut:  $\omega_0 = \frac{1}{RC} = 2\pi f_0$  tel que  $f_0 = \frac{1}{2\pi RC} = 10^3$  Hz  
 $G_0 = 20 \log \left( \frac{R_1 + R_2}{R_1} \right) = 3dB$   $G_0 = 20 \log (1 + \frac{R_2}{R_1}) = 10 \log 2$   $\Rightarrow \left( \frac{R_2}{R_1} \right)^2 = 2$

$RC = \frac{1}{2\pi \cdot 10^3}$   
 $\frac{R_2}{R_1} = \sqrt{2} - 1$

$\rightarrow \begin{cases} \text{si } R = 10k\Omega & C \approx 1,6 \cdot 10^{-8} F = 16 nF \\ \text{si } R_1 = 10k\Omega & R_2 = 4,1 k\Omega \end{cases}$

(\*) Si on ne pense pas à  $\log 2 = 0,3 \rightarrow \log (1 + \frac{R_2}{R_1}) = \frac{3}{20} \rightarrow \frac{R_2}{R_1} = 10^{\frac{3}{20}} - 1$